



10 - BJT Advanced

Name: _____


In-Class Problems

(1) Consider the simple RC network shown below. Which of the following is true or false:


(a) This simple $\tau=RC$ network charges up as v'_{be} is applied according to: $v_{be} = v'_{be}(1 - e^{-t/\tau})$ and discharges as $v_{be} = v'_{be}e^{-t/\tau}$.

(b) RC time constant (τ) is the time required to charge the capacitor, through the resistor, by ≈ 63.2 percent of the difference between the initial value and final value, and is the time required to discharge the capacitor to ≈ 36.8 percent ($1/e$).

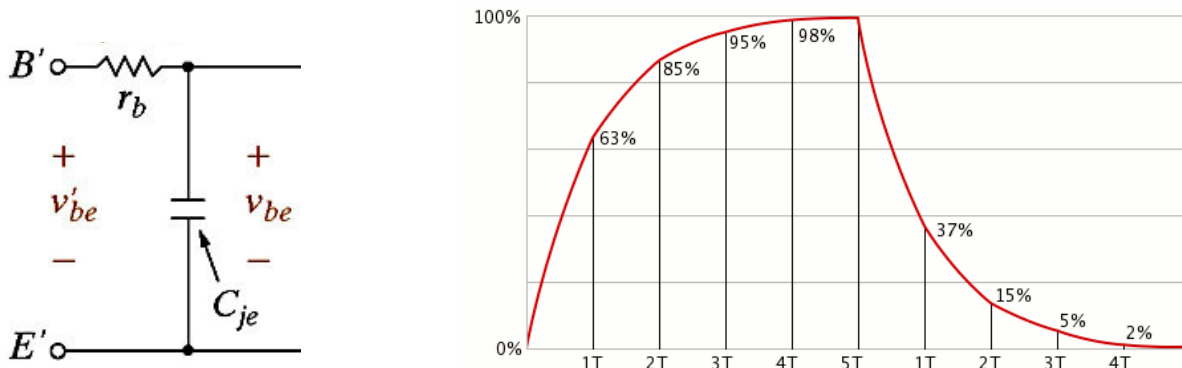(c) Cutoff frequency for input into this simple network would be calculated as: $f_c(\text{Hz}) = \frac{1}{2\pi RC} = \frac{1}{2\pi\tau}$





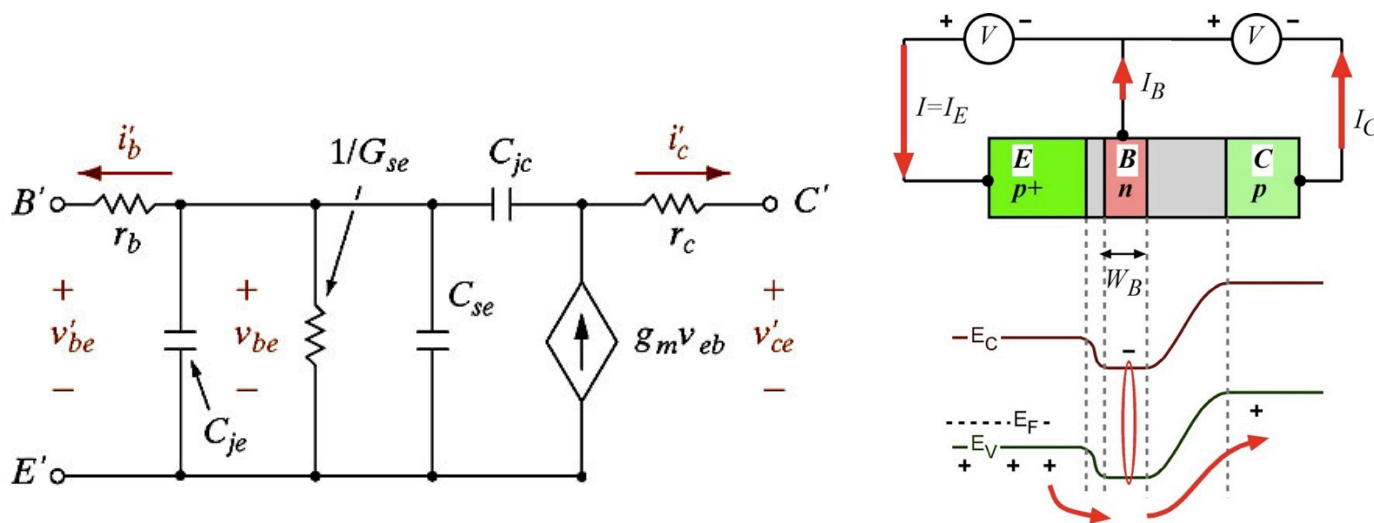(2) Now... a BJT is even more complex! So lets examine the hybrid-Pi circuit shown below.



- (a) why for the circuit do we have a base resistance? *Hint, think of base geometry and doping level.*
- (b) why for the circuit do we have a collector resistance but no emitter resistance?
- (c) Which is larger, C_{je} or C_{jc} ? Why? Brief answer, this is easy!
- (d) C_{se} is for forward bias (storage or diffusion capacitance), and typically dominates over the reverse bias capacitance (depletion capacitance), and is calculated based on classic parallel plate capacitance or based on $C=dQ/dV$?
- (e) We only have C_{se} for the base-emitter, not for the base-collector because the base-collector is reverse biased (no dQ for a dV across the base-collector). True or false?
- (f) The $1/G_{se}$ resistor, what are the units for G_{se} ? This is easy.
- (g) The $1/G_{se}$, with ONE word (one semiconductor term), explain what it represents.
- (h) The g_m term, with ONE word (one term), explain what it is called, and give its units (should make sense, given how voltage is transformed into current by it).
- (i) The g_m term, linearly turns emitter-base voltage into collector current. For the DC model of the BJT it was not linear with voltage but was exponential with voltage. Draw a diode characteristic and explain why the small-signal AC input voltage is approximated in this circuit to provide a linear increase in collector output current.
- (j) The hybrid-Pi circuit is the small-signal (AC) model for the case where DC bias is applied and the BJT is in normal forward active mode (amplification). If the EB junction were reverse biased instead of normal forward bias, cross-out the components that should be removed to show what an incoming AC signal at the B would see.
- (k) For a fixed I_B , you keep increasing V_{CE} and see the effect of base narrowing. Which components in the diagram will change? **FOUR OF THEM SHOULD CHANGE!**

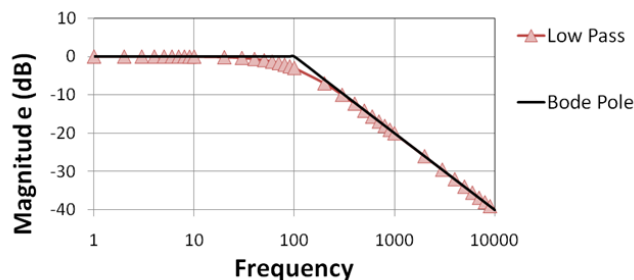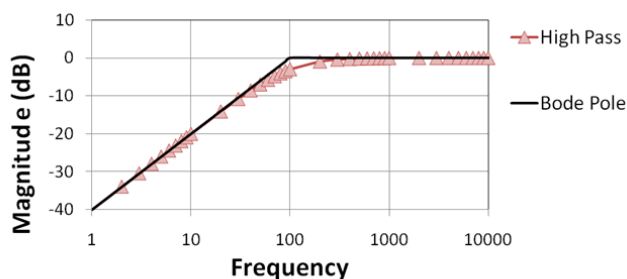(3) Lets look at the frequency response of a semiconductor amplifier from an even simpler standpoint that you deal with in electronics. Here are Bode plots for generic high-pass and low-pass circuits.





(a) This should be easy. If you were creating a Bode plot for a stand-alone BJT using the Hybrid Pi model, which would you be more concerned with, the high-pass or low-pass Bode plot?

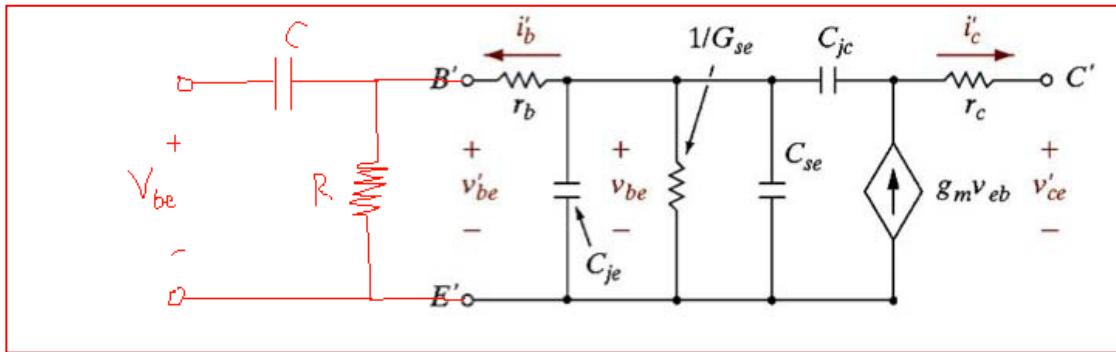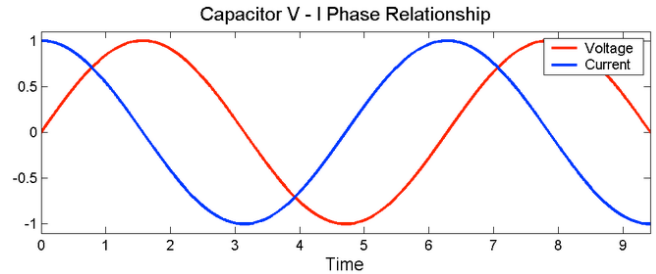(b) This should be easy too. Lets say you wanted to filter out very low frequencies as well coming into your BJT. You achieve this by adding only two components to the hybrid-Pi model as shown below, but it does not work. What is the problem w/ this setup? *Hint: think of the DC conditions needed to setup the BJT for high-frequency AC amplification.*



$$Z = R + \frac{1}{j\omega C}$$

$$\omega = 2\pi f \quad j \text{ because } \frac{\pi}{2} \text{ phase shift}$$



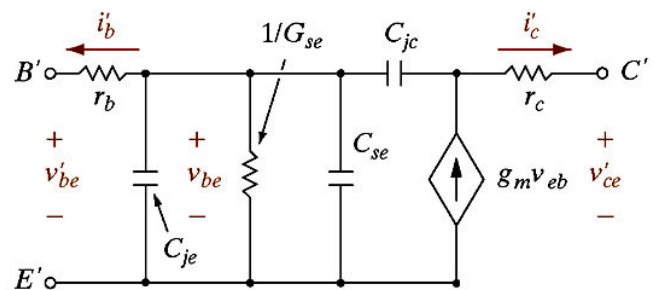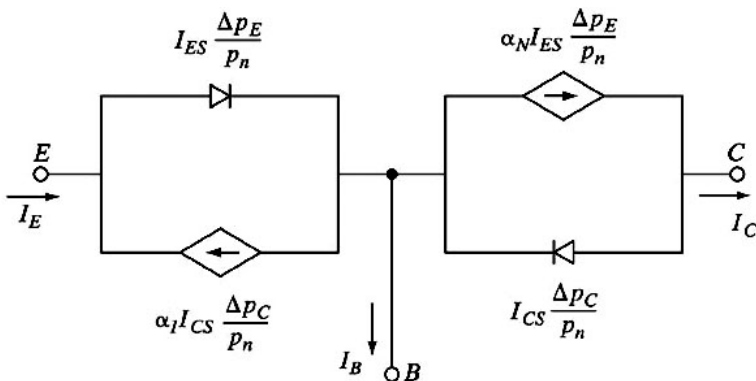(4) Two models are shown below, one on the left, and one on the right. I will generally refer to them that way. So here are some tougher questions to see who really knows their stuff!

$$\Delta p_E = p_n (e^{qV_{EB}/kT} - 1)$$



(a) Draw a diagram, only one diagram, and mark/annotated it, to explain why for the model at left the current sources are exponential with voltage and why in the model at right the current sources are linear with voltage.

(b) Redraw the model on the right, for a NPN BJT operating in inverse mode (opposite of normal forward active mode). Make sure you list out everything you see in the model, components, voltages, and currents!

**** at this point you can stop and go over problems for the old test, or you can do this last problem which is also good review for the test ****

(5) Whew, your LAST calculations for a PNP BJT, some review basically...

| | <i>Emitter</i> | <i>Base</i> | <i>Collector</i> |
|-----------------------|-------------------------------|-----------------------------|-----------------------------|
| $W_b = 0.2 \mu m$ | $N_a = 5 \times 10^{18} / cc$ | $N_d = 10^{16} / cc$ | $N_a = 10^{15} / cc$ |
| $Area = 10^{-4} cm^2$ | $\tau_n = 100 ps$ | $\tau_p = 2500 ps$ | $\tau_n = 2 \mu s$ |
| | $\mu_p = 100 cm^2 / V - s$ | $\mu_n = 1500 cm^2 / V - s$ | $\mu_p = 450 cm^2 / V - s$ |
| | $\mu_n = 150 cm^2 / V - s$ | $\mu_p = 400 cm^2 / V - s$ | $\mu_n = 1500 cm^2 / V - s$ |

(a) First, some easy review. As shown in the parameters above, why does carrier lifetime increase from emitter, to base, to collector?

(b) Some more easy review.

- Calculate L_n in the emitter and L_p in the base, based on doping L_n should be significantly less than L_p !
- Also, please comment on L_p compared to W_b , and why that is important for BJT operation.